

YEAR 9 SCIENCE **PHYSICAL SCIENCES** **INVESTIGATION 10.10 - Ohm's Law**

Perform the following investigation about the relationship between voltage and resistance.

Use a light globe and a ceramic resistor - do two investigations and have two tables of results.

Change the voltage from 2 V to 12 V - record your data as you go.

INVESTIGATION 10.10

Changing resistance


AIM To investigate the relationship between voltage and resistance of a light globe

Materials:

power supply (variable) switch
 9-volt light globe and holder ammeter
 6 connecting leads with voltmeter
 alligator clips or banana plugs

METHOD AND RESULTS

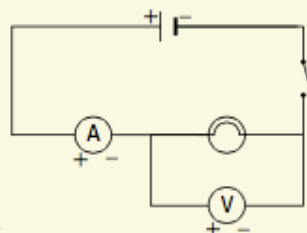- Set up the circuit shown in the diagram on the right and leave the switch open.



- Construct a table like the one below in which to record your measurements of the electric current flowing through the light globe, the voltage drop across the globe and the calculated resistance.
- Set the power supply to 2 volts.
- Close the switch and quickly read the meters, recording the electric current and voltage drop in your table. Ensure that the electric current is recorded in amperes (not milliamperes).
- With the switch closed, set the power supply to 4 volts.
- Quickly measure and record the electric current and voltage displayed on the meters.
- Set the power supply to 6 volts (again not opening the switch) and

quickly measure and record the electric current and voltage displayed on the meters.

- Calculate the resistance of the globe for each of the three power supply settings and record them in your table.
- Plot a graph of voltage drop (V) versus electric current (I) for the light globe.
- Repeat the experiment, constructing a new table in which to record your data. This time, however, start with the power supply set to 6 volts. Then decrease it to 4 volts and then 2 volts.
- Plot a second graph of the voltage drop versus electric current on the same set of axes as the first graph in a different colour.

DISCUSS AND EXPLAIN

- Does the resistance increase or decrease during the first part of the experiment, when the power supply setting is being increased?
- How is the change in resistance different during the second part of the experiment, when the power supply setting is being decreased?
- What changing property of the filament do you think caused the resistance of the light globe to change?
- Explain any difference between the shape of the first graph and that of the second graph.

The characteristics of a light globe

Power supply setting (volts)	Electric current (amperes)	Voltage drop (volts)	Resistance (ohms)
2			
4			
6			