 
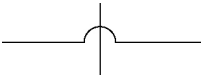


Simple circuits

Student: Class:

Circuit components


1. Complete the table by identifying the component or drawing the symbol for the named component.

Name	Symbol	Name	Symbol
Ammeter			
		Battery	
		Cell	
Voltmeter			


Drawing simple circuits

2. Use the symbols for the circuit components to draw the equivalent circuit for each example.

(a)

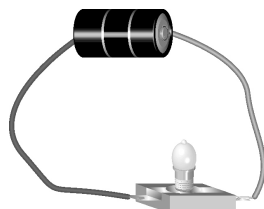

(b)

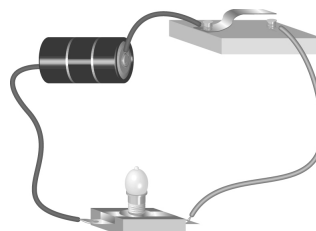

The torch circuit

3. Draw a circuit diagram to show how a torch works.

